

# ECE-249

## CA-2

Name - Amit Kumar Anand

Registration No - 12315581

Section - K23PG


Roll No - 34

Subject - ECE-249(CA-2)



**Q1.** Apply the Thevenin and Norton theorem to find the value of Current across 4 Ohm, if the input applied voltage is the last two digits of your registration number.

**\*\*Verify the simulation result with theoretical result.**

**\*\* (Example: If your registration is 12315216 then Input supply is 16 V and if last two digit is zero then Input supply is 10 V.**

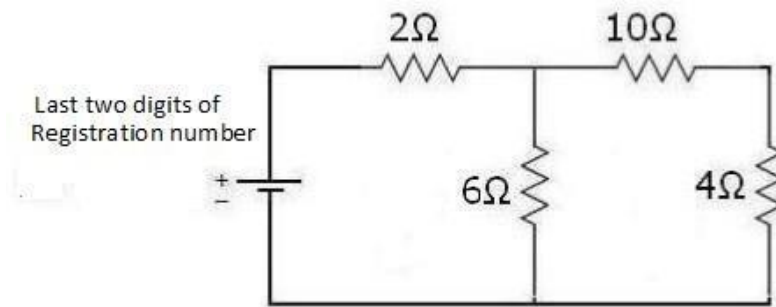


**ANSWER 1 -**

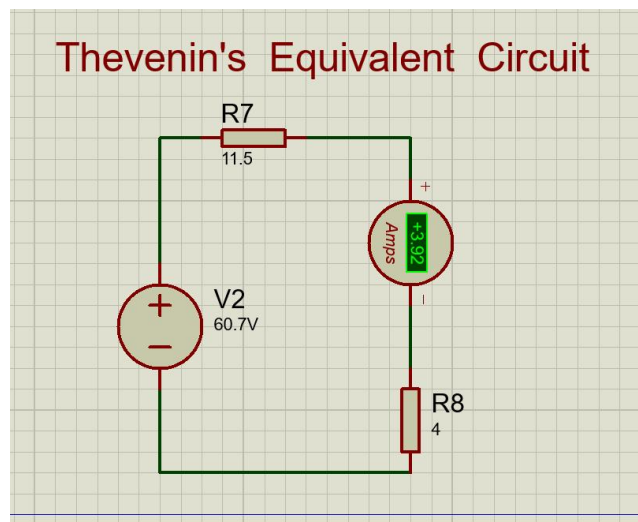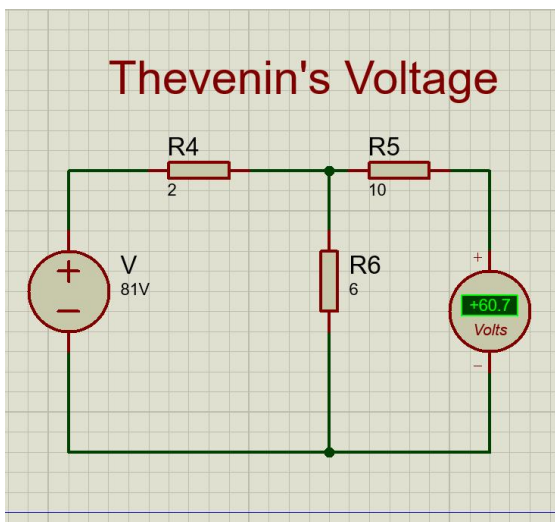


Thevenin's Theorem

Registration no - 12315581

$$\therefore \boxed{V = 81 \text{ V}}$$

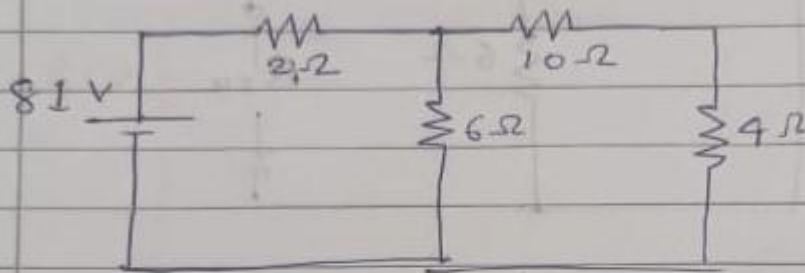

$R_L = 4 \Omega$  (given)

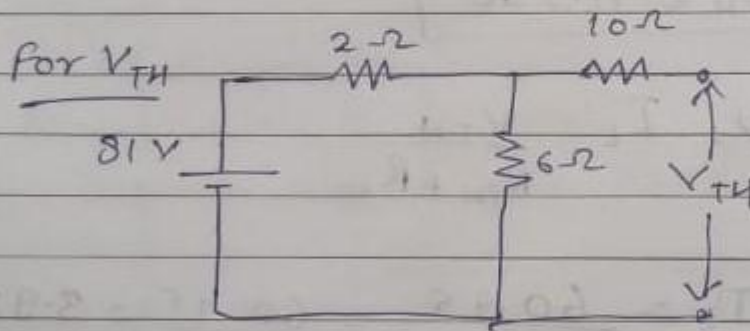

$$\frac{V_{TH} - 81}{2} + \frac{V_{TH}}{6} = 0$$


$$3(V_{TH} - 81) + V_{TH} = 0$$

$$4V_{TH} - 243 = 0$$

$$\therefore \boxed{V_{TH} = \frac{243}{4} = 60.75}$$

Now, For  $R_{TH}$

Remove all voltage sources

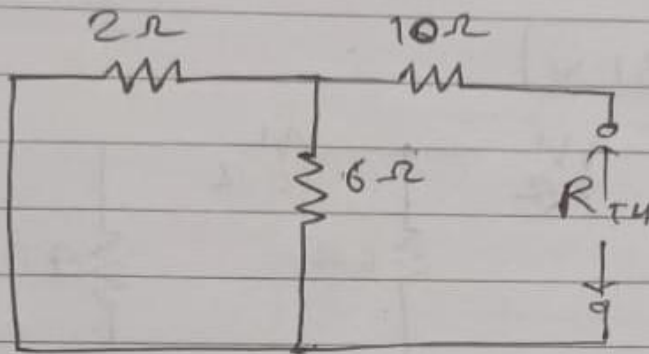

$$R_{TH} = 10 + \left( \frac{2 \times 6}{2 + 6} \right) = 10 + \frac{12}{8} = 10 + 1.5$$


$$\boxed{R_{TH} = 11.5 \Omega}$$

$$\text{Now, } I_L = \frac{V_{TH}}{R_{TH} + R_L}$$


$$I_L = \frac{60.75}{11.5 + 4} = \frac{60.75}{15.5} = 3.92 \text{ A}$$

$$\boxed{I_L = 3.92 \text{ A}}$$

# Norton's Equivalent Circuit

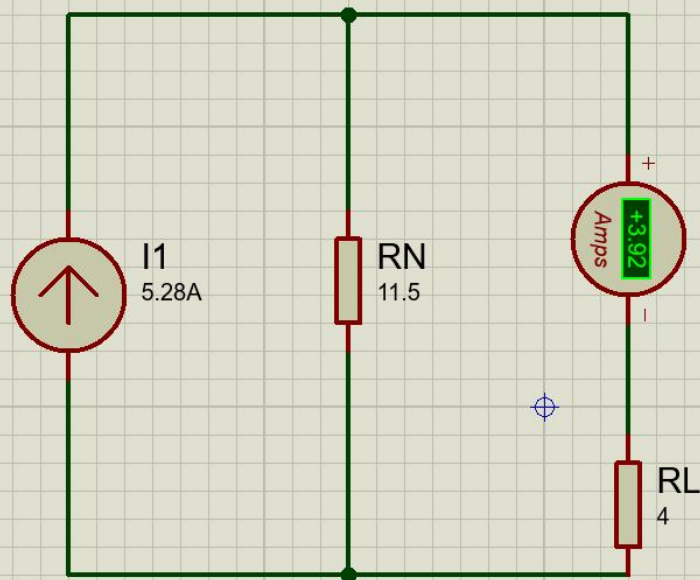


# Norton's Current

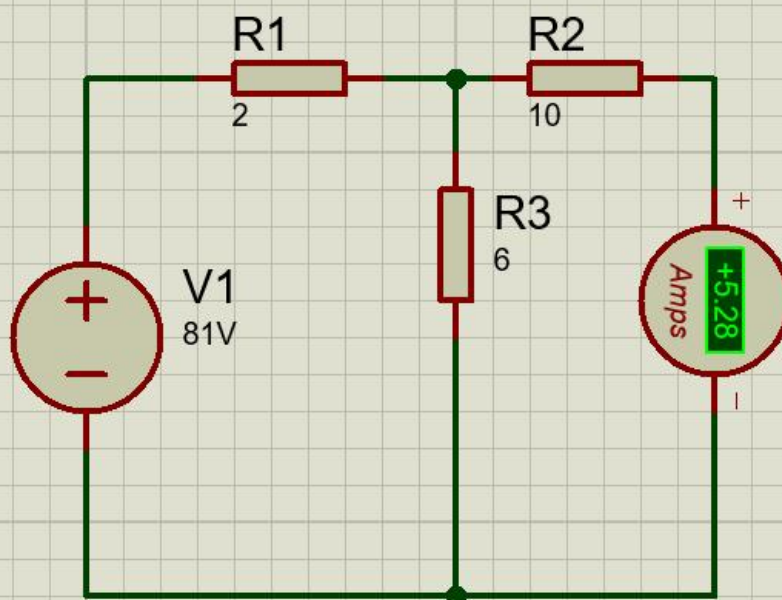

## Norton's Theorem


Registration no. - 12315581

$\therefore V = 81 \text{ V}$

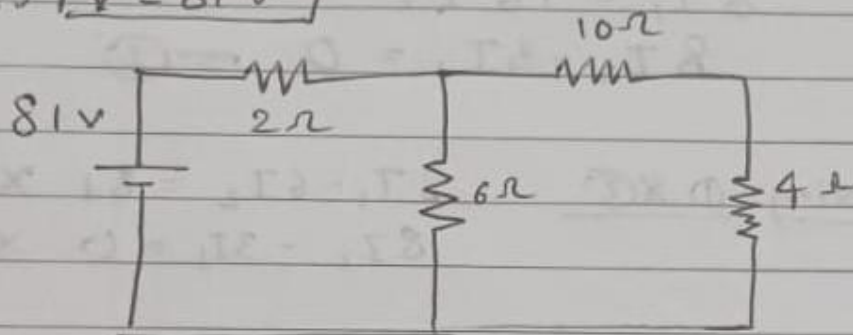

$R_L = 4\Omega$  (given)

for  $I_N$

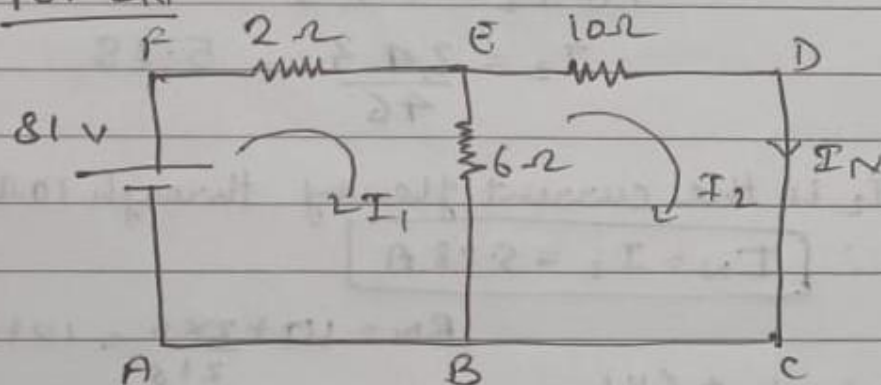

Applying KVL in loop ABEP :

$$81 - 2I_1 - 6(I_1 - I_2) = 0$$

$$81 - 2I_1 - 6I_1 + 6I_2 = 0$$

$$8I_1 - 6I_2 = 81 \quad \text{--- (1)}$$

Applying KVL in loop BCDE

$$6(I_1 - I_2) - 10I_2 = 0$$

$$6I_1 - 6I_2 - 10I_2 = 0$$

$$6I_1 = 16I_2$$

$$8I_2 - 3I_1 = 0 \quad \text{--- (2)}$$

Solving (1) & (2)

$$8I_1 - 6I_2 = 81 \times 3$$

$$8I_2 - 3I_1 = 0 \times 8$$

$$24I_1 - 18I_2 = 243$$

$$-24I_1 + 64I_2 = 0$$

$$46I_2 = 243$$

$$I_2 = \frac{243}{46} = 5.28$$


As,  $I_2$  is the current flowing through  $10\Omega$  resistor-

$$\therefore I_N = I_2 = 5.28 \text{ A}$$

$$R_N = 10 + \frac{2 \times 6}{2+6} = 10 + 1.5$$

Norton's Equivalent Ckt.

$$R_N = 11.5 \Omega$$

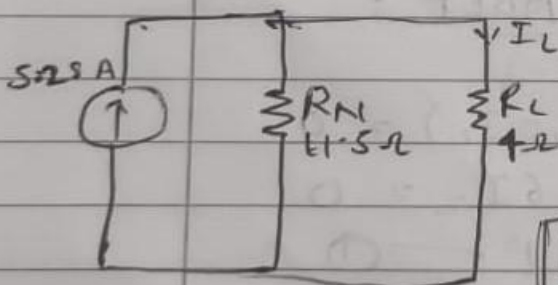

$$\therefore I_L = \frac{I_N R_N}{R_N + R_L} = \frac{5.28 \times 11.5}{11.5 + 4}$$

$$I_L = \frac{60.75}{15.5} = 3.92 \text{ A}$$

**Q2.** Implementation of a Boolean function using 4:1 multiplexer on proteus software. The Minterms will be implementation of Decimal to octal conversion of your registration number.

**\*\***For example: if your registration is (12315532)<sub>10</sub> (assume it is in decimal) and the octal conversion of this is (56765614)<sub>8</sub>. Then you need to implement last 4 digit start from LSB. Now you need to implement 5614 according to example given. So, implement ( $\sum$ , ) =  $\sum$ (, ,, ) using 4:1 Multiplexer.

**\*\*\***Also implementing number does not repeat twice. For example registration is 12315534, and octal conversion will be 56765616. In this case 6 is repeating twice. So, you need to take the next MSB, like 7, 5,1, 6. Implement ( $\sum$ , ) =  $\sum$ (,, , ) using 4:1 Multiplexer.

**ANSWER 2 -**



Registration no : 12315581

Decimal to Octal Conversion of Reg no.

8	1 2 3 1 5 5 8 1	5
8	15 39 44 7	7
8	19 24 30	6
8	24 05 3	5
8	30 06	6
8	37 5	7
8	46	6
	5	

$$(12315581)_{10} = (56765675)_8$$

So, for min term we have to take last 4 digits of octal numbers (i.e. 5675) but 5 is repeating so we are taking 0 another min term.



$$\text{So, } F(A, B, C) = \sum (0, 5, 6, 7)$$



	00	01	10	11
$\bar{A}$	0	1	2	3
A	4	5	6	7
	$\bar{A}$	A	A	A

• Bulb will be glow at (0, 5, 6, 7)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



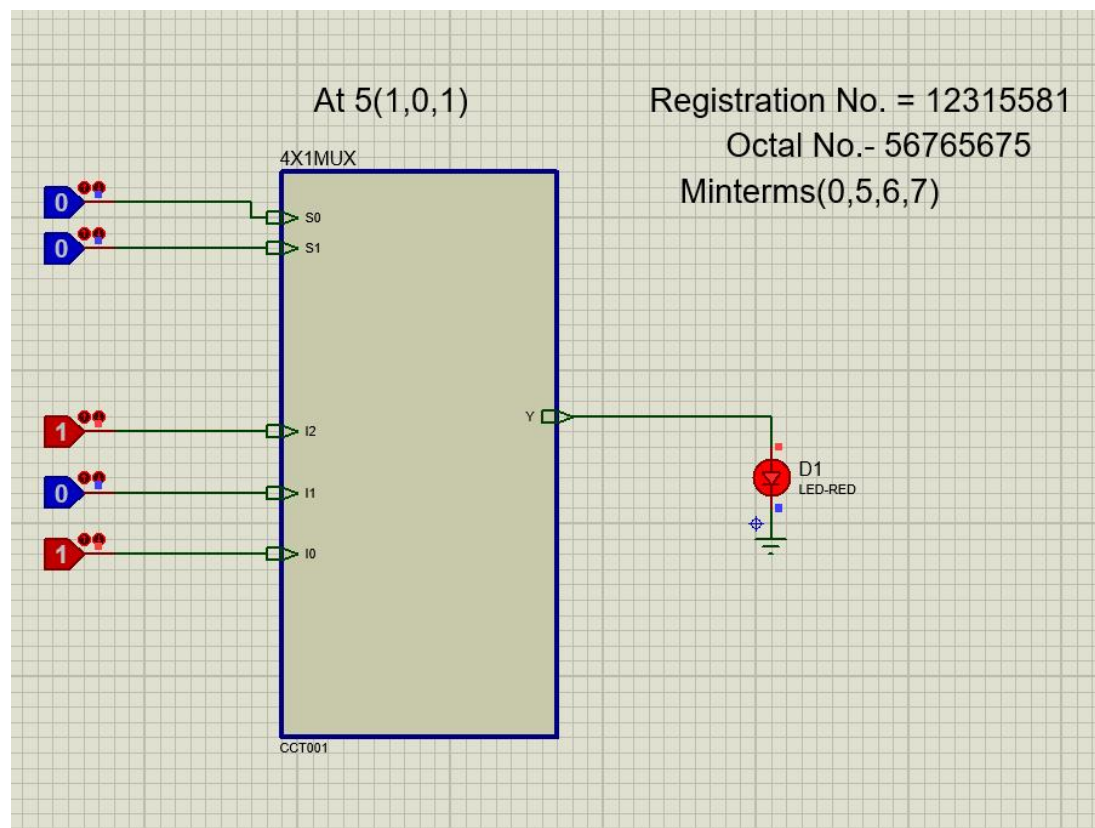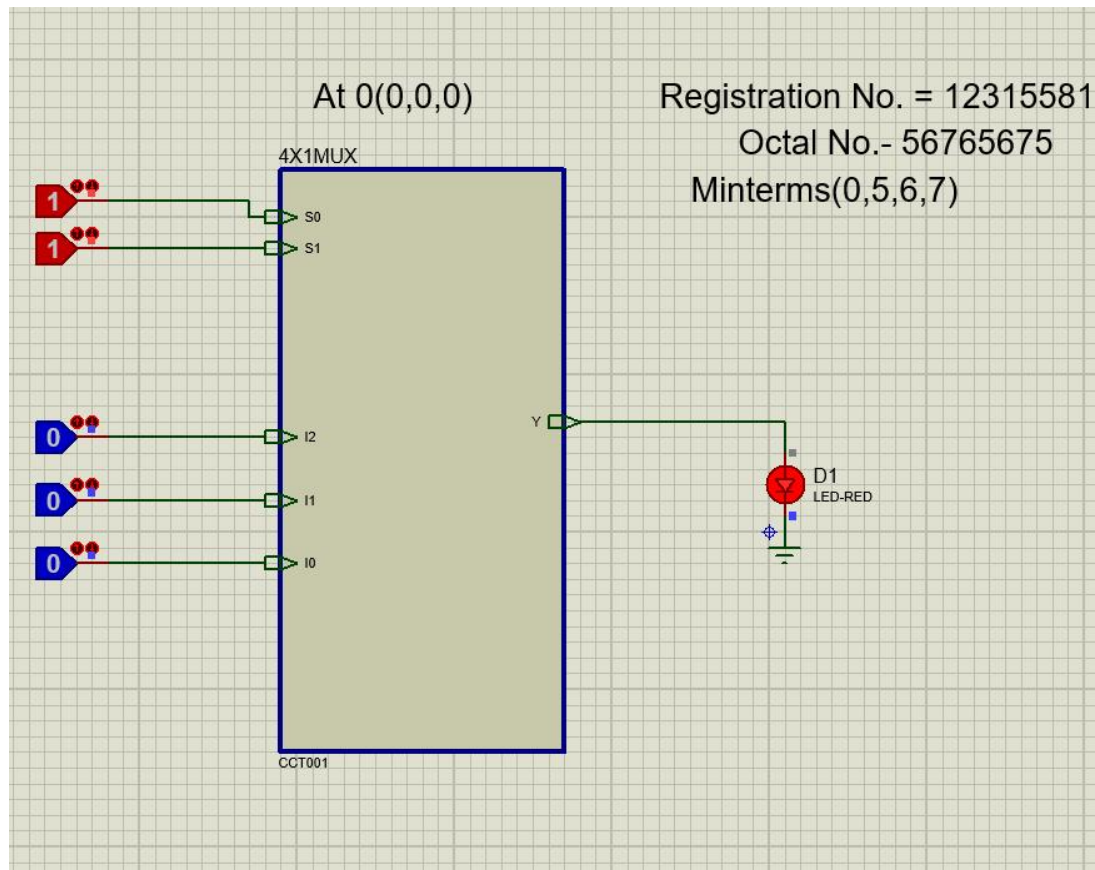

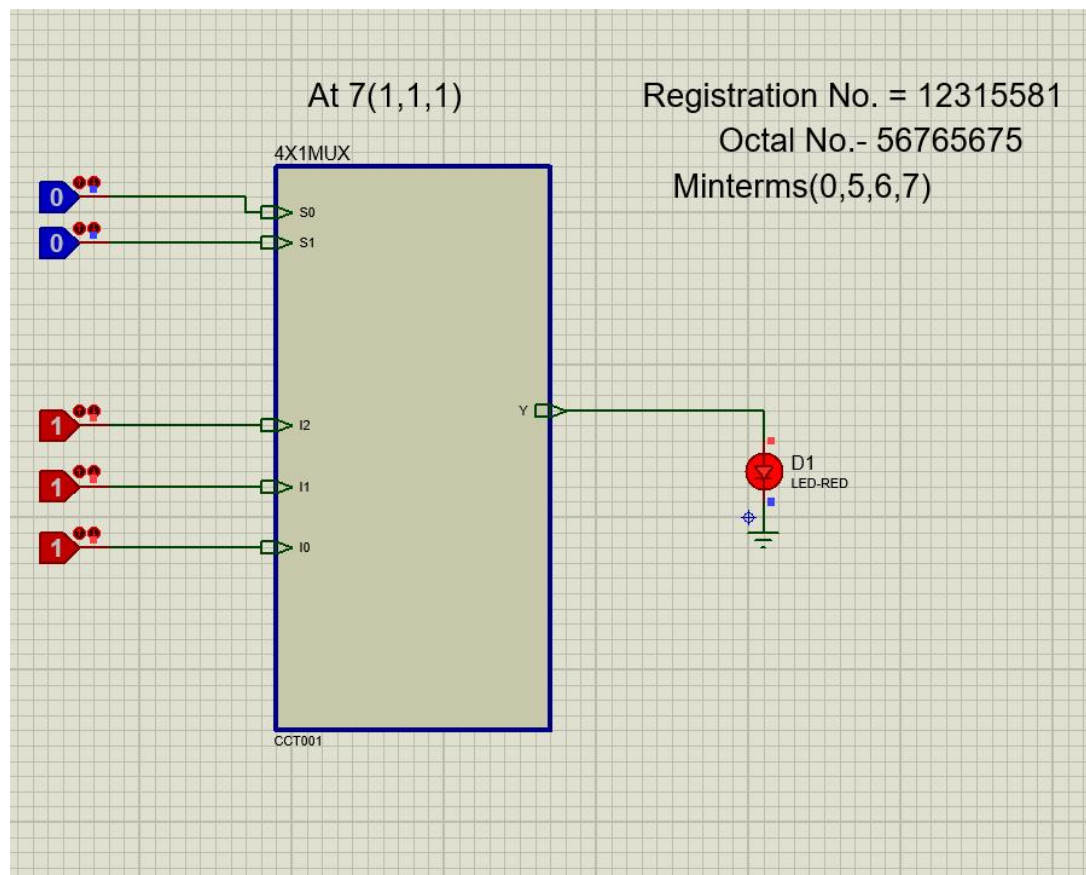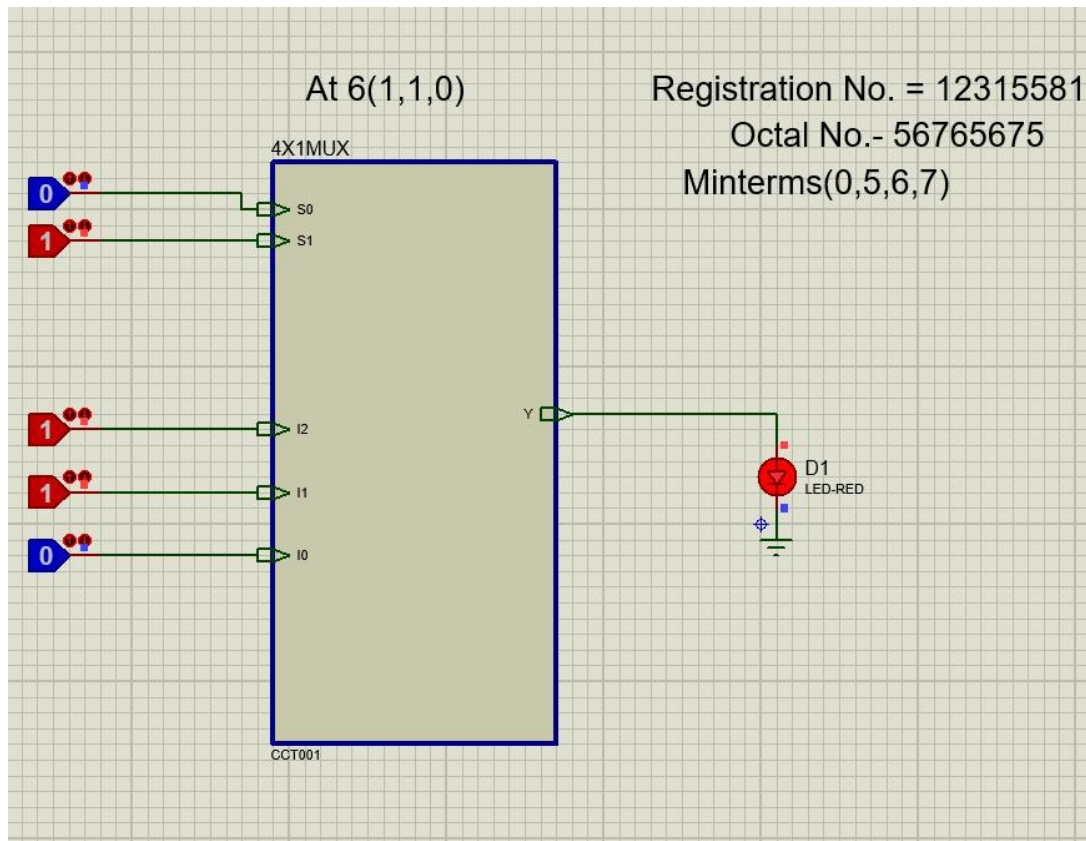


**Q.3.** Interfacing of IR sensor with an Arduino on Proteus. Note: You need to connect IR sensor on pin no. (Last digit of your registration no. and LED will be connected on pin no. 10).

**\*\***For example- if your registration no is 12315532, IR sensor will be connected on pin no. 2. If according to registration number last digit is 0 or 1 then consider input of IR to pin no. 5.

**\*\*\***Display your name and registration on virtual screen if obstacle detected otherwise display your roll number

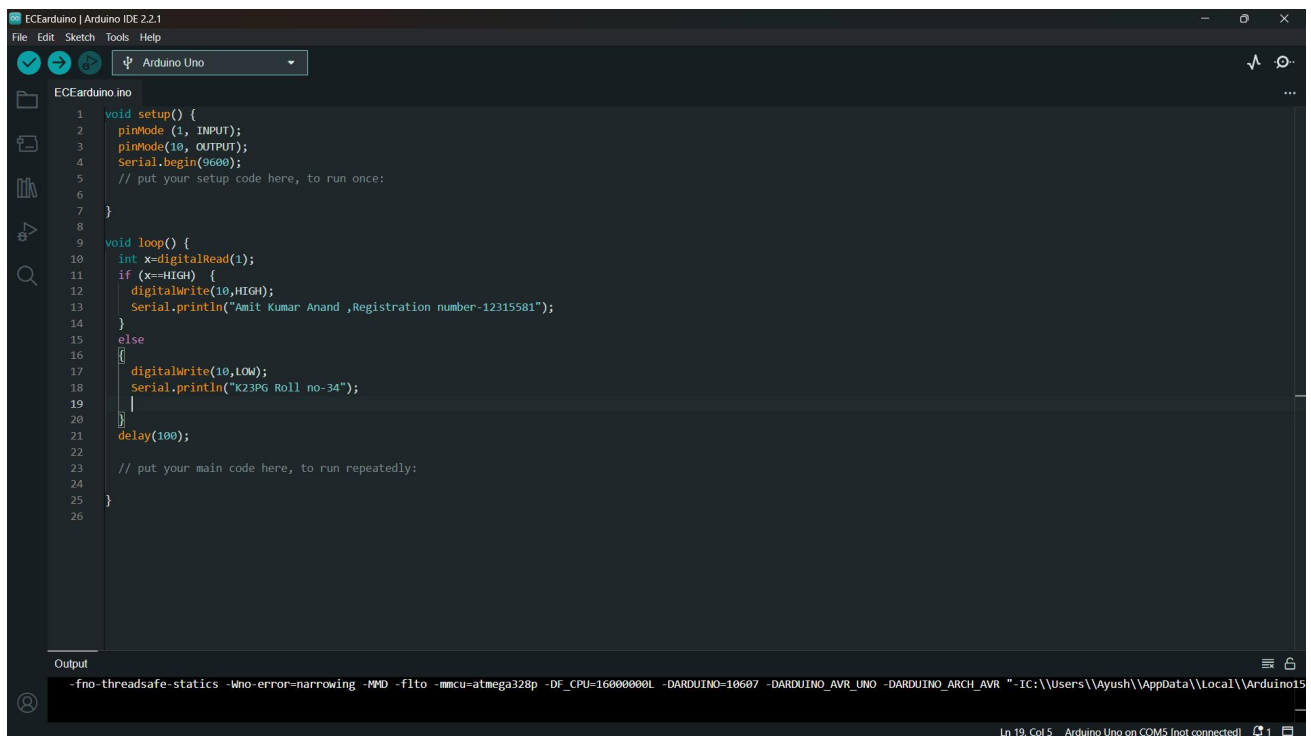**ANS:- WHEN THERE IS NO OBSTACLE (TOGGLE=0)  
ROLL NO IS PRINTED IN VIRTUAL TERMINAL**



```
1 void setup() {
2   pinMode(1, INPUT);
3   pinMode(10, OUTPUT);
4   Serial.begin(9600);
5   // put your setup code here, to run once:
6
7 }
8
9 void loop() {
10  int x=digitalRead(1);
11  if (x==HIGH) {
12    digitalWrite(10,HIGH);
13    Serial.println("Amit Kumar Anand ,Registration number-12315581");
14  }
15  else
16  {
17    digitalWrite(10,LOW);
18    Serial.println("K23PG Roll no-34");
19  }
20  delay(100);
21
22  // put your main code here, to run repeatedly:
23
24 }
25
26
```

Output

-fno-threadsafe-statics -Wno-error=narrowing -std=c++11 -fno-rtti -mmcu=atmega328p -DF\_CPU=16000000L -DARDUINO=10607 -DARDUINO\_AVR\_UNO -DARDUINO\_ARCH\_AVR -IC:\\Users\\Ayush\\AppData\\Local\\Arduino15

Ln 19, Col 5 Arduino Uno on COM5 [not connected]

